

Drawdio

Name _____

Step 1
Switch, battery,
and status LED

Step 2
Piezo (speaker)
and duty cycle indicator LEDs

Step 3
555 timer and supporting electronics,
alligator clips

